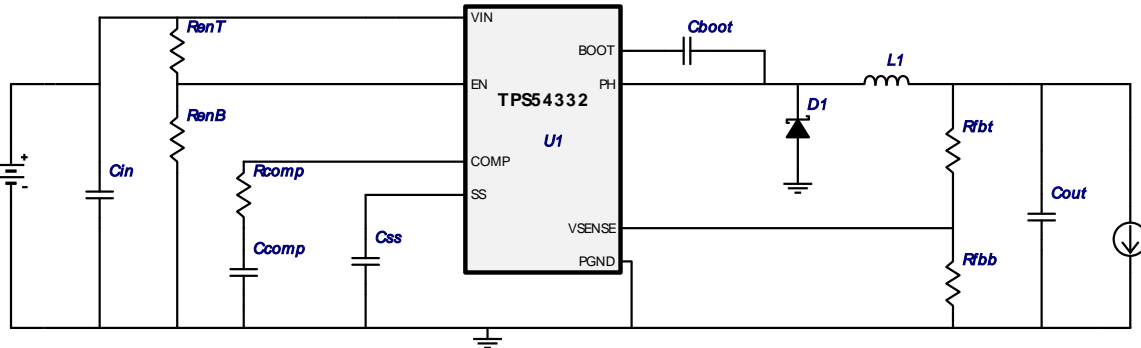


WEBENCH® Design Report

 Design : 1214885/21 TPS54332DDA
 TPS54332DDA 10.0V-27.0V to 5.0V @ 1.5A

Electrical BOM

#	Name	Manufacturer	Part Number	Quantity	Price	Properties	Footprint
1.	Cboot	Kemet	C0603C104K3RACTU Series= X7R	1	\$0.01	Cap= 100.0 nF VDC= 25.0 V IRMS= 0.0 A	0603 10mm2
2.	Ccomp	MuRata	GRM1885C1H182JA01D Series= C0G/NP0	1	\$0.02	Cap= 1.8 nF VDC= 50.0 V IRMS= 0.0 A	0603 10mm2
3.	Cin	TDK	C5750X7R1H106M Series= X7R	1	\$0.68	Cap= 10.0 µF ESR= 3.0 mOhm VDC= 50.0 V IRMS= 5.5 A	2220 60mm2
4.	Cout	MuRata	GRM21BR60J226ME39L Series= X5R	1	\$0.05	Cap= 22.0 µF ESR= 9.0 mOhm VDC= 6.3 V IRMS= 3.5 A	0805 13mm2
5.	Css	TDK	C1608C0G1E103J Series= C0G/NP0	1	\$0.07	Cap= 10.0 nF VDC= 25.0 V IRMS= 0.0 A	0603 10mm2
6.	D1	Diodes Inc.	B240A-13-F	1	\$0.09	VF@Io= 500.0 mV VRRM= 40.0 V	SMA 37mm2
7.	L1	Bourns	SRN6045-100M	1	\$0.18	L= 10.0 µH DCR= 58.6 mOhm	SRN6045 64mm2
8.	Rcomp	Panasonic	ERJ3EKF1802V Series= CUSTOM	1	\$0.01	Res= 18.0 kOhm Power= 100.0 mW Tolerance= 1%	CUSTOM 10mm2
9.	RenB	Panasonic	ERJ3EKF1802V Series= CUSTOM	1	\$0.01	Res= 18.0 kOhm Power= 100.0 mW Tolerance= 1.0%	CUSTOM 10mm2
10.	RenT	Multicomp	MC0603SAF1053T5E Series= CUSTOM	1	\$0.10	Res= 105.0 kOhm Power= 100.0 mW Tolerance= 1.0%	CUSTOM 10mm2
11.	Rfbb	Vishay-Dale	CRCW040210K0FKED Series= CRCW..e3	1	\$0.01	Res= 10.0 kOhm Power= 63.0 mW Tolerance= 1.0%	0402 8mm2
12.	Rfbt	Vishay-Dale	CRCW040253K6FKED Series= CRCW..e3	1	\$0.01	Res= 53.6 kOhm Power= 63.0 mW Tolerance= 1.0%	0402 8mm2

#	Name	Manufacturer	Part Number	Quantity	Price	Properties	Footprint
13.	U1	Texas Instruments	TPS54332DDA	1	\$1.40	Switcher	MPDS092E 57mm2

Operating Values

#	Name	Value	Category	Description
1.	BOM Count	13.0		Total Design BOM count
2.	Total BOM	\$2.641		Total BOM Cost
3.	Cin IRMS	461.896 m A	Current	Input capacitor RMS ripple current
4.	Cout IRMS	127.31 m A	Current	Output capacitor RMS ripple current
5.	IC Ipk	1.721 A	Current	Peak switch current in IC
6.	Iin Avg	327.57 m A	Current	Average input current
7.	L Ipp	441.015 m A	Current	Peak-to-peak inductor ripple current
8.	M1 Irms	671.593 m A	Current	Q lavg
9.	FootPrint	361.0 mm2	General	Total Foot Print Area of BOM components
10.	Frequency	1000.0 k Hz	General	Switching frequency
11.	IC Tolerance	28.0 m V	General	IC Feedback Tolerance
12.	M Vds Act	63.268 m V	General	Voltage drop across the MosFET
13.	Mode	CCM	General	Conduction Mode
14.	Pout	7.5 W	General	Total output power
15.	D1 Tj	44.991 degC	Op_Point	D1 junction temperature
16.	Vout OP	5.0 V	Op_Point	Operational Output Voltage
17.	Cross Freq	61.073 k Hz	Op_point	Bode plot crossover frequency
18.	Duty Cycle	20.046 %	Op_point	Duty cycle
19.	Efficiency	84.799 %	Op_point	Steady state efficiency
20.	IC Tj	59.948 degC	Op_point	IC junction temperature
21.	ICThetaJA	50.0 degC/W	Op_point	IC junction-to-ambient thermal resistance
22.	IOUT_OP	1.5 A	Op_point	Iout operating point
23.	Phase Marg	101.888 deg	Op_point	Bode Plot Phase Margin
24.	VIN_OP	27.0 V	Op_point	Vin operating point
25.	Vout p-p	7.783 m V	Op_point	Peak-to-peak output ripple voltage
26.	Cin Pd	640.043 μ W	Power	Input capacitor power dissipation
27.	Cout Pd	145.87 μ W	Power	Output capacitor power dissipation
28.	Diode Pd	599.654 m W	Power	Diode power dissipation
29.	IC Pd	598.96 m W	Power	IC power dissipation
30.	L Pd	145.035 m W	Power	Inductor power dissipation
31.	Total Pd	1.344 W	Power	Total Power Dissipation

Design Inputs

#	Name	Value	Description
1.	Iout	1.5 A	Maximum Output Current
2.	Iout1	1.5 Amps	Output Current #1
3.	VinMax	27.0 V	Maximum input voltage
4.	VinMin	10.0 V	Minimum input voltage
5.	Vout	5.0 V	Output Voltage
6.	Vout1	5.0 Volt	Output Voltage #1
7.	base_pn	TPS54332	Texas Instruments base part number
8.	Ta	30.0 degC	Ambient temperature

Design Assistance

1. **TPS54332** Product Folder : <http://www.ti.com/product/tps54332> : contains the data sheet and other resources.

Texas Instruments' WEBENCH simulation tools attempt to recreate the performance of a substantially equivalent physical implementation of the design. Simulations are created using Texas Instruments' published specifications as well as the published specifications of other device manufacturers. While Texas Instruments does update this information periodically, this information may not be current at the time the simulation is built. Texas Instruments does not warrant the accuracy or completeness of the specifications or any information contained therein. Texas Instruments does not warrant that any designs or recommended parts will meet the specifications you entered, will be suitable for your application or fit for any particular purpose, or will operate as shown in the simulation in a physical implementation. Texas Instruments does not warrant that the designs are production worthy.

You should completely validate and test your design implementation to confirm the system functionality for your application prior to production.

Use of Texas Instruments' WEBENCH simulation tools is subject to [Texas Instruments' Site Terms and Conditions of Use](#). Prototype boards based on WEBENCH created designs are provided AS IS without warranty of any kind for evaluation and testing purposes and are subject to the terms of the [Evaluation License Agreement](#).